

*Numerical on BJT*

## Problem #1

- In a common base connection,  $I_E = 1\text{mA}$ ,  $I_C = 0.95\text{mA}$ . Calculate the value of  $I_B$

## Solution

Using the relation,

$$I_E = I_B + I_C$$

$$1 = I_B + 0.95$$

$$I_B = 1 - 0.95 = \mathbf{0.05\text{ mA}}$$

## Problem #2

- In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

## Solution

$$\text{Here, } \alpha = 0.9, \quad I_E = 1 \text{ mA}$$

$$\text{Now} \quad \alpha = \frac{I_C}{I_E}$$

$$\text{or} \quad I_C = \alpha I_E = 0.9 \times 1 = 0.9 \text{ mA}$$

$$\text{Also} \quad I_E = I_B + I_C$$

$$\therefore \quad \text{Base current, } I_B = I_E - I_C = 1 - 0.9 = \mathbf{0.1 \text{ mA}}$$

## Problem #3

In a common base connection,  $I_C = 0.95 \text{ mA}$  and  $I_B = 0.05 \text{ mA}$ .  
Find the value of  $\alpha$ .

Solution:

$$\text{We know } I_E = I_B + I_C = 0.05 + 0.95 = 1 \text{ mA}$$

$$\therefore \text{ Current amplification factor, } \alpha = \frac{I_C}{I_E} = \frac{0.95}{1} = \mathbf{0.95}$$

## Problem #4

**In a common base connection, the emitter current is 1mA. If the emitter circuit is open, the collector current is 50  $\mu$ A. Find the total collector current. Given that  $\alpha = 0.92$**




Solution:

$$\text{Here, } I_E = 1 \text{ mA, } \alpha = 0.92, \quad I_{CBO} = 50 \mu\text{A}$$

$$\begin{aligned} \therefore \quad \text{Total collector current, } I_C &= \alpha I_E + I_{CBO} = 0.92 \times 1 + 50 \times 10^{-3} \\ &= 0.92 + 0.05 = \mathbf{0.97 \text{ mA}} \end{aligned}$$
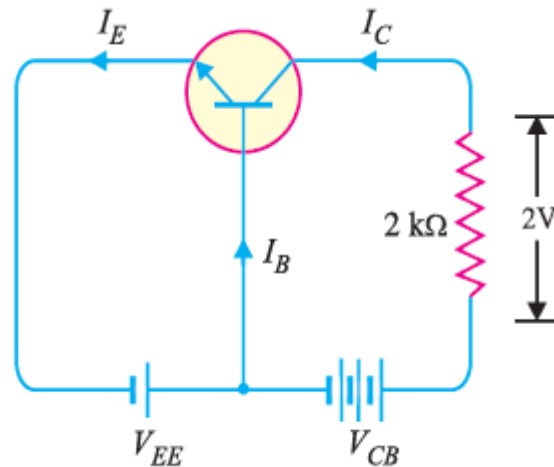
## Problem #5

In a common base connection,  $\alpha = 0.95$ . The voltage drop across  $2\text{ k}\Omega$  resistance, which is connected in the collector is  $2\text{V}$ . Find the base current.



Solution:

The voltage drop across RC ( $= 2 \text{ k}\Omega$ ) is 2V.

$$\begin{aligned} \therefore I_C &= 2 \text{ V} / 2 \text{ k}\Omega = 1 \text{ mA} \\ \text{Now } \alpha &= I_C / I_E \end{aligned}$$


$$\therefore I_E = \frac{I_C}{\alpha} = \frac{1}{0.95} = 1.05 \text{ mA}$$

Using the relation,  $I_E = I_B + I_C$

$$\begin{aligned} \therefore I_B &= I_E - I_C = 1.05 - 1 \\ &= \mathbf{0.05 \text{ mA}} \end{aligned}$$
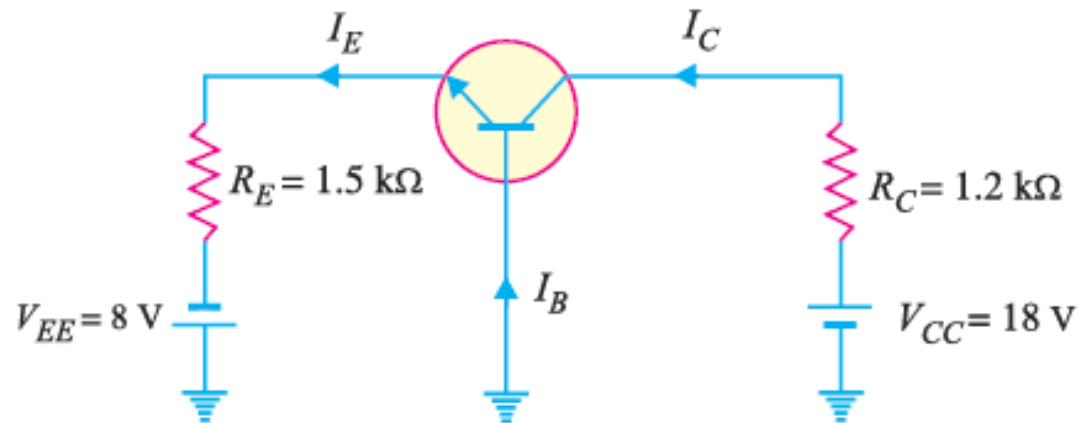
## Problem #6

- For the common base circuit shown in Figure, determine  $I_C$  and  $V_{CB}$ . Assume the transistor to be of silicon.



## Solution:

Since the transistor is of silicon,  $V_{BE} = 0.7V$ .

Applying Kirchhoff's voltage law to the emitter-side loop, we get,

$$\begin{aligned} V_{EE} &= I_E R_E + V_{BE} \\ \text{or } I_E &= \frac{V_{EE} - V_{BE}}{R_E} \\ &= \frac{8V - 0.7V}{1.5 \text{ k}\Omega} = 4.87 \text{ mA} \\ \therefore I_C \simeq I_E &= \mathbf{4.87 \text{ mA}} \end{aligned}$$

Applying Kirchhoff's voltage law to the collector-side loop, we have,

$$\begin{aligned} V_{CC} &= I_C R_C + V_{CB} \\ \therefore V_{CB} &= V_{CC} - I_C R_C \\ &= 18 \text{ V} - 4.87 \text{ mA} \times 1.2 \text{ k}\Omega = \mathbf{12.16 \text{ V}} \end{aligned}$$

## Problem #7

Find the value of  $\beta$  if (i)  $\alpha = 0.9$  (ii)  $\alpha = 0.98$  (iii)  $\alpha = 0.99$ .

Solution:

(i)  $\alpha = 0.9$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{1-0.9} = 9$$

(ii)  $\alpha = 0.98$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = 49$$

(iii)  $\alpha = 0.99$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$$

## Problem #8

**Calculate  $I_E$  in a transistor for which  $\beta = 50$  and  $I_B = 20 \mu\text{A}$ .**



Solution:

$$\text{Here } \beta = 50, \quad I_B = 20\mu\text{A} = 0.02 \text{ mA}$$

Now


$$\beta = \frac{I_C}{I_B}$$

$$\therefore I_C = \beta I_B = 50 \times 0.02 = 1 \text{ mA}$$

$$\text{Using the relation, } I_E = I_B + I_C = 0.02 + 1 = \mathbf{1.02 \text{ mA}}$$
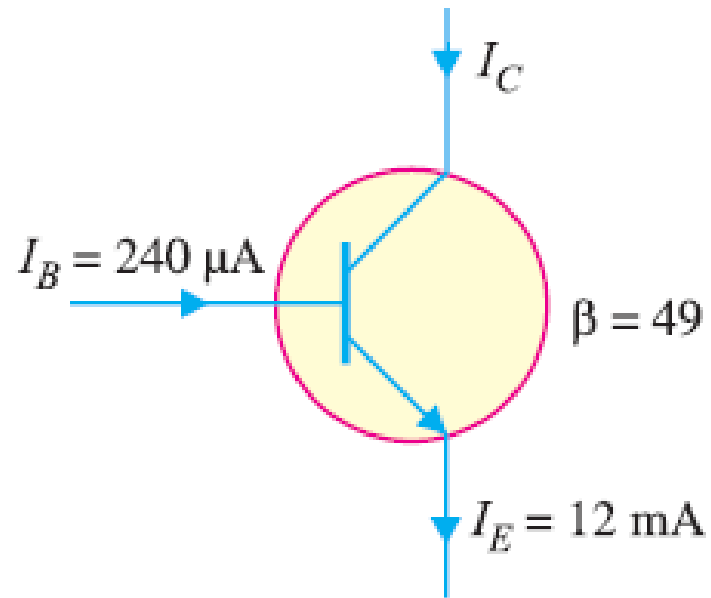
## Problem #9

Find the  $\alpha$  rating of the transistor shown in Figure. Hence determine the value of  $I_C$  using both  $\alpha$  and  $\beta$  rating of the transistor.



Solution:

$$\alpha = \frac{\beta}{1 + \beta} = \frac{49}{1 + 49} = \mathbf{0.98}$$


The value of  $I_C$  can be found by using either  $\alpha$  or  $\beta$  rating as under :

$$I_C = \alpha I_E = 0.98 (12 \text{ mA}) = \mathbf{11.76 \text{ mA}}$$

$$\text{Also } I_C = \beta I_B = 49 (240 \text{ }\mu\text{A}) = \mathbf{11.76 \text{ mA}}$$
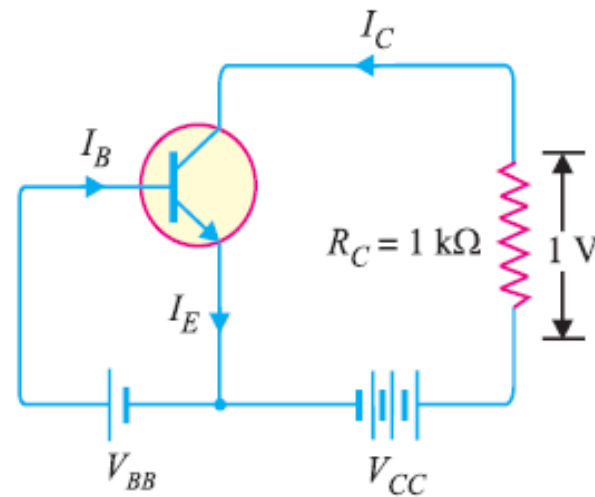
## Problem #10

For a transistor,  $\beta = 45$  and voltage drop across  $1\text{k}\Omega$  which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.



## Solution:

The voltage drop across RC (= 1 kΩ) is 1 volt.


$$\therefore I_C = \frac{1\text{ V}}{1\text{ k}\Omega} = 1\text{ mA}$$

Now 
$$\beta = \frac{I_C}{I_B}$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{1}{45} = \mathbf{0.022\text{ mA}}$$
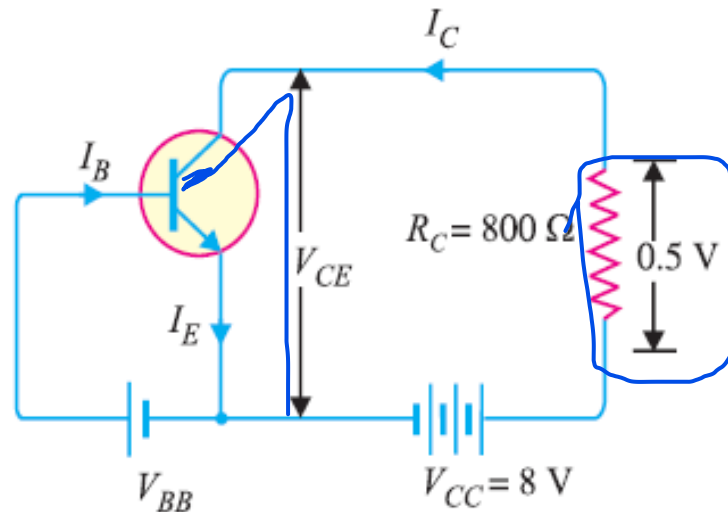
## Problem #11

A transistor is connected in common emitter (CE) configuration in which collector supply is 8 V and the voltage drop across resistance  $R_C$  connected in the collector circuit is 0.5 V. The value of  $R_C = 800\ \Omega$ . If  $\alpha = 0.96$ , determine : (i) collector-emitter voltage (ii) base current.



(i)

Collector-emitter voltage,

$$V_{CE} = V_{CC} - 0.5 = 8 - 0.5 = \mathbf{7.5\text{ V}}$$

(ii)

The voltage drop across  $R_C (= 800\ \Omega)$  is 0.5 V.

$$I_C = \frac{0.5\text{ V}}{800\ \Omega} = \frac{5}{8}\text{ mA} = 0.625\text{ mA}$$

$$\text{Now } \beta = \frac{\alpha}{1 - \alpha} = \frac{0.96}{1 - 0.96} = 24$$

$$\therefore \text{Base current, } I_B = \frac{I_C}{\beta} = \frac{0.625}{24} = \mathbf{0.026\text{ mA}}$$

### **Problem #12**

**In a transistor,  $I_B = 68 \mu\text{A}$ ,  $I_E = 30 \text{ mA}$  and  $\beta = 440$ .**

**Determine the  $\alpha$  rating of the transistor. Then determine the value of  $I_C$  using both the  $\alpha$  rating and  $\beta$  rating of the transistor.**



Solution:

$$\alpha = \frac{\beta}{\beta + 1} = \frac{440}{440 + 1} = \mathbf{0.9977}$$

$$I_C = \alpha I_E = (0.9977) (30 \text{ mA}) = \mathbf{29.93 \text{ mA}}$$

$$I_C = \beta I_B = (440) (68 \text{ }\mu\text{A}) = \mathbf{29.93 \text{ mA}}$$